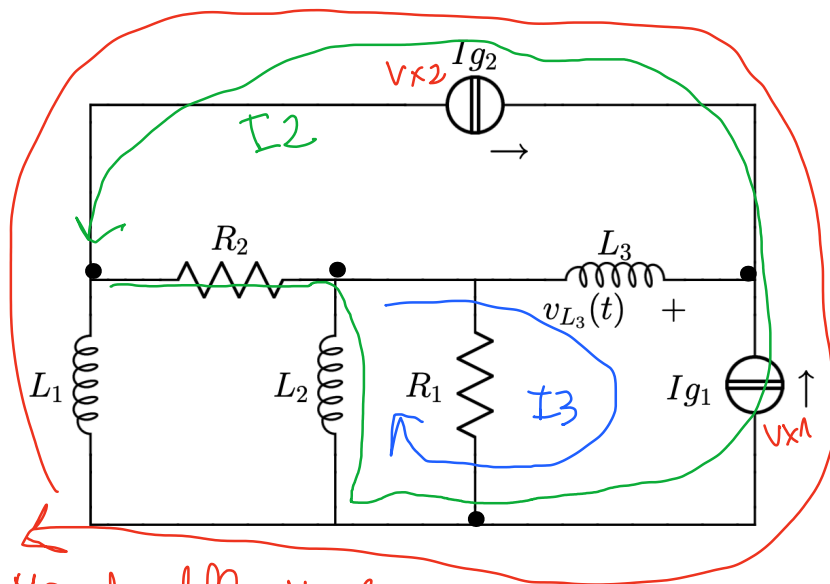


Parallelo Maglie


venerdì 1 agosto 2025 15:55

Risolvere il circuito in figura

I_1


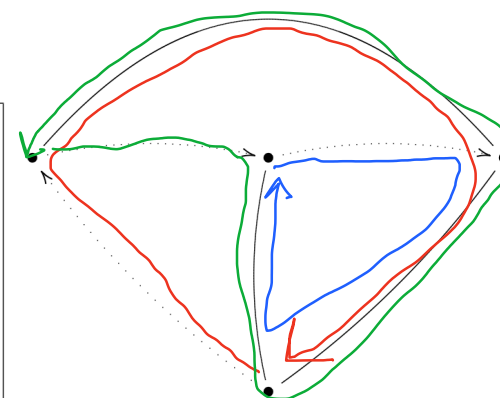
$$\begin{aligned} L_1 &= 1 \\ R_1 &= 1 \\ L_2 &= \frac{1}{2} \\ \mathbf{I}_{g1} &= -1 + j \\ R_2 &= 2 \\ L_3 &= 2 \\ \mathbf{I}_{g2} &= -1 + j \\ \omega &= 1 \end{aligned}$$



Metodo delle Maglie.

$$Y_a = \frac{1}{j\omega L_2} + \frac{1}{R_1} = \frac{1}{j1} + \frac{1}{1} = \frac{2}{5} + 1 = -25 + 1 \quad (\text{RISOLTO IL PARALLELO}).$$

$$Z_a = \frac{1}{-25 + 1} \cdot \frac{1 + 25}{1 + 25} = \frac{1 + 25}{5} = \frac{1}{5} + \frac{2}{5}j$$

$$\begin{bmatrix} j\omega L_1 & 0 & 0 \\ 0 & R_2 + Z_a & -Z_a \\ 0 & -Z_a & Z_a + j\omega L_3 \end{bmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} -V_{x1} + V_{x2} \\ V_{x1} - V_{x2} \\ -V_{x1} \end{pmatrix}$$

— √ ' √ /

$$\begin{cases} (5\omega L_1)I_1 = -V_{x1} + V_{x2} \\ (R_2 + Z_a)I_2 - Z_a I_3 = +V_{x1} - V_{x2} \\ -Z_a I_2 + (Z_a + 5\omega L_3)I_3 = -V_{x1} \\ I_2 - I_3 - I_1 = I_{q1} \\ I_1 - I_2 = I_{q2} \end{cases}$$

Risoluzione.

$$\begin{cases} 5I_1 = -V_{X1} + V_{X2} \\ \left(2 + \frac{1}{5} + \frac{2}{5} 5\right) I_2 + \left(-\frac{1}{5} - \frac{2}{5} 5\right) I_3 = +V_{X1} - V_{X2} \\ \left(-\frac{1}{5} - \frac{2}{5} 5\right) I_2 + \left(\frac{1}{5} + \frac{2}{5} 5 + 25\right) I_3 = -V_{X1} \end{cases}$$

$$\left\{ \begin{array}{l} 5(5-1+I_2) = -V_{X1} + V_{X2} \\ \left(\frac{11}{5} + \frac{2}{5}5\right)I_2 + \left(-\frac{1}{5} - \frac{2}{5}5\right)I_3 = +V_{X1} - V_{X2} \\ \left(-\frac{1}{5} - \frac{2}{5}5\right)I_2 + \left(\frac{1}{5} + \frac{12}{5}5\right)I_3 = -V_{X1} \\ I_2 - I_3 + 1 - 5 - I_2 = -145 \end{array} \right. \rightarrow \left\{ \begin{array}{l} -1 - 5 + 5I_2 = -V_{X1} + V_{X2} \\ \left(\frac{11}{5} + \frac{2}{5}5\right)I_2 + \left(-\frac{1}{5} - \frac{2}{5}5\right)I_3 = +V_{X1} - V_{X2} \\ \left(-\frac{1}{5} - \frac{2}{5}5\right)I_2 + \left(\frac{1}{5} + \frac{12}{5}5\right)I_3 = -V_{X1} \\ -I_3 + 1 - 5 = -145 \rightarrow I_3 = -25 + 2 \\ I_1 = 5 - 1 + I_2 \end{array} \right.$$

$$I_1 = 3 - 1 + I_2$$

NOTA

→

$$I_2 - I_3 - I_1 = -1 + 3$$

$$I_2 + 23 - 2 - 3 + 1 - I_2 = -1 + 3$$

I_2 È UN PARAMETRO LIBERO.

$$I_2 = 1$$

$$1 + 23 - 2 - I_1 = -1 + 3$$

$$-I_1 = -1 + 3 - 1 - 23 + 2$$

$$I_1 = 1 - 3 + 1 + 23 - 2$$

$$I_1 = 3$$

ho 2 equazioni e 3 incognite, quindi una variabile è libera per forza.

$$\begin{cases} -1 - 3 + 3I_2 = -Vx_1 + Vx_2 \\ \left(\frac{11}{5} + \frac{2}{5}3\right)I_2 + \left(-\frac{1}{5} - \frac{2}{5}3\right)I_3 = +Vx_1 - Vx_2 \\ \left(-\frac{1}{5} - \frac{2}{5}3\right)I_2 + \left(\frac{1}{5} + \frac{12}{5}3\right)I_3 = -Vx_1 \end{cases} \rightarrow$$

$$\begin{cases} -1 - 3 + 3 = -Vx_1 + Vx_2 \\ \frac{11}{5} + \frac{2}{5}3 + \left(-\frac{1}{5} - \frac{2}{5}3\right)(-23 + 2) = +Vx_1 - Vx_2 \\ -\frac{1}{5} - \frac{2}{5}3 + \left(\frac{1}{5} + \frac{12}{5}3\right)(-23 + 2) = -Vx_1 \end{cases}$$

$$\rightarrow \begin{cases} -Vx_1 + Vx_2 = -1 \\ \frac{11}{5} + \frac{2}{5}3 + \frac{1}{5} - \frac{2}{5}3 = -\frac{2}{5} - 4 - \frac{4}{5} = -1 + Vx_1 - Vx_2 \end{cases}$$

$$\begin{cases} 43 + 3 - 43 - 6 = -1 \rightarrow -1 = -1 \checkmark \\ Vx_2 = -43 - 6 \end{cases}$$

$$\left\{ \begin{array}{l} -\frac{1}{5} - \frac{2}{5} + \frac{2}{5} + \frac{24}{5} + \frac{24}{5} = -V \times 1 \\ V \times 1 = -65 - 5 \end{array} \right.$$

quindi, il sistema dà luogo ai seguenti risultati

$$\left\{ \begin{array}{l} V \times 1 = -45 - 5 \\ V \times 2 = -45 - 6 \\ I_1 = 3 \\ I_2 = 1 \\ I_3 = 2 - 25 \end{array} \right.$$

$$V \times 2 = -45 - 6$$

$$I_1 = 3$$

$$I_2 = 1$$

$$L3 = 2 - 25$$

BILANCIO DI POTENZA

$$\mathbb{I}R_2 = \mathbb{I}2 \approx 1$$

$$\text{Tr } A + \text{Tr } B = -I_2 + I_3 = -1 + 2 - 2j = 1 - 2j$$

$$T_{L3} = T_3 = 2.25$$

$$I_{L1} = I_1 = 3$$

$$I_{q2} = -1 + 5 \text{ (Note)}$$

$$I_{q1} = -1 + 3 \text{ (Note)}$$

$$F_{R1} = \frac{V_{R1}}{R_1} = 1$$

$$V_{R2} = R2 \cdot I_{R2} = 2 \cdot 1 = 2$$

$$V_{R1} = V_{L2} = Z_a \cdot (I_{R1} + I_{L2}) = 1$$

$$V_{L3} = j\omega L_3 \cdot I_{L3} = 25(2 - 25) = 45 + j9$$

$$VL1 = 5uL1 \cdot 1L1 = 3 \cdot 3 = -1$$

$$V_{g1} = V_{x1} = -45 - 3$$

$$V_{g2} = V_{x2} = -65 - 6$$

$$I_{L2} = \frac{V_{L2}}{j\omega L2} = \frac{1}{\frac{1}{2}j} = \frac{2}{j} = -2j$$

$$P_{Cg2} = \frac{1}{2} V_{g2} I_{g2}^* = \frac{1}{2} (-4j - 6) (-1 - j) = (-2j - 3) (-1 - j) = 2j - 2 + 3 + 3j = 5j + 1$$

$$P_{Cg1} = \frac{1}{2} V_{g1} I_{g1}^* = \frac{1}{2} (-4j - 5) (-1 - j) = (-2j - \frac{5}{2}) (-1 - j) = 2j - 2 + \frac{5}{2} + \frac{5}{2}j = \frac{9}{2}j + \frac{1}{2}$$

$$P_{R1} = \frac{1}{2} R1 |I_{R1}|^2 = \frac{1}{2} 1 = \frac{1}{2}$$

$$P_{R2} = \frac{1}{2} R2 |I_{R2}|^2 = \frac{1}{2} 2 \cdot 1 = 1$$

$$\frac{1+1}{2} = 1 + \frac{1}{2}$$

$$Q_{L1} = \frac{1}{2} \omega L1 |I_{L1}|^2 = \frac{1}{2} 1 = \frac{1}{2}$$

$$Q_{L2} = \frac{1}{2} \omega L2 |I_{L2}|^2 = \frac{1}{2} \frac{1}{2} 4 = 1$$

$$Q_{L3} = \frac{1}{2} \omega L3 |I_{L3}|^2 = \frac{1}{2} 2 \cdot 8 = 8$$

$$P_{Rg1} = \text{Im}(P_{Cg1}) = \frac{9}{2}$$

$$P_{Rg2} = \text{Im}(P_{Cg2}) = 5$$

$$\frac{1}{2} + 1 + 8 = \frac{9}{2} + 5$$

$$\frac{19}{2} = \frac{19}{2}$$

